

WELCOME TO MY PRESENTATION

Presented by

- Name: Kawsar Ahmed
 - ID: 12105297
 - Program: BSEEE

Presentation Topic:

- Half Wave Rectifier
- Full Wave Rectifier





Crystal Diode Rectifiers

- Rectifier: Rectifier is that circuit, that converts ac to dc.

- The following two types of rectifier circuit can be used:
 - I. Half wave rectifier
 - II. Full wave rectifier

Half wave Rectifier

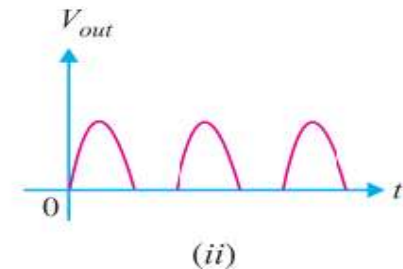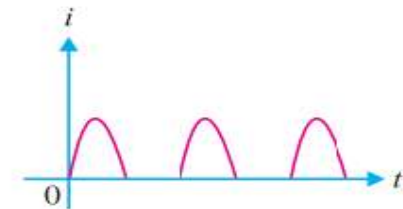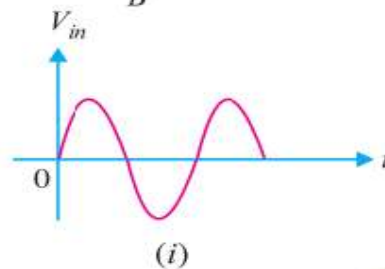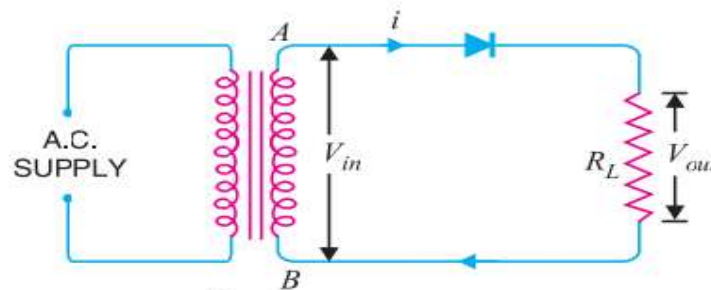- The process of removing one-half the input signal to establish a dc level is called *half-wave rectification*.
- In Half wave rectification, the rectifier conducts current during positive half cycle of input ac signal only.
- Negative half cycle is suppressed.







Half wave Rectifier

➤ AC voltage across secondary terminals AB changes its polarity after each half cycle.

➤ During negative half cycle terminal A is negative so diode is reversed biased and conducts no current.

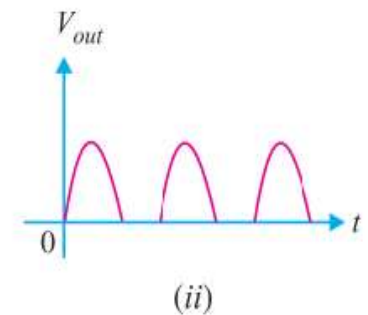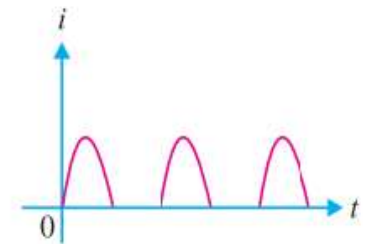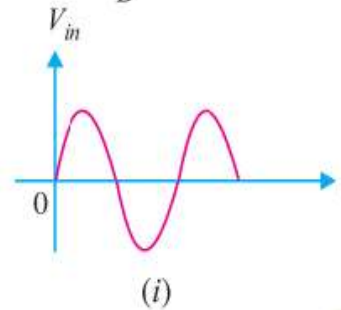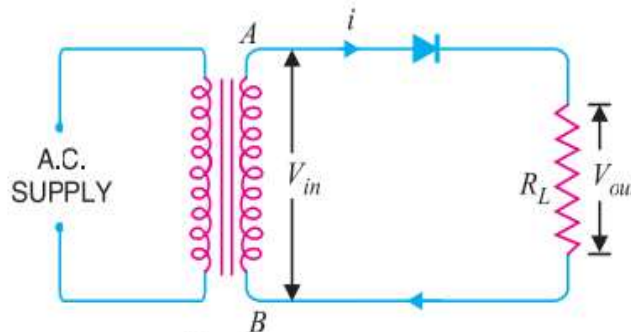➤ So, current flows through diode during positive half cycle only.



➤ In this way current flows through load R_L in one direction

Half wave Rectifier

- Disadvantage of Half wave rectifier:
 - The pulsating current in output contains ac components whose frequency is equal to supply frequency so filtering is needed.
 - The ac supply delivers power during half cycle only so output is low.


Half wave Rectifier

□ Output frequency of HWR:

➤ Output frequency of HWR is equal to input frequency.

➤ This means when input ac completes one cycle, rectified wave also completes one cycle.


$$f_{out} = f_{in}$$

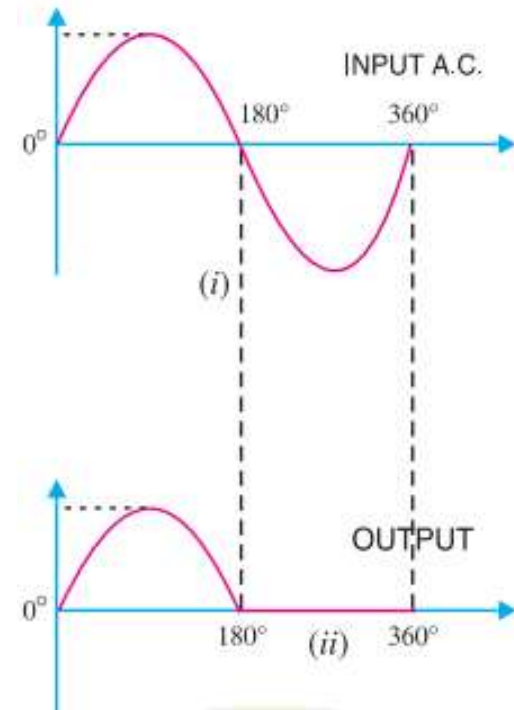

Full-Wave Rectifier



- In Full wave rectification current flow through the load in same direction for both half cycle of input ac.
- This can be achieved with two diodes working alternatively.
- For one half cycle one diode supplies current to load and for next half cycle another diode works.

Centre Tap Full Wave Rectifier

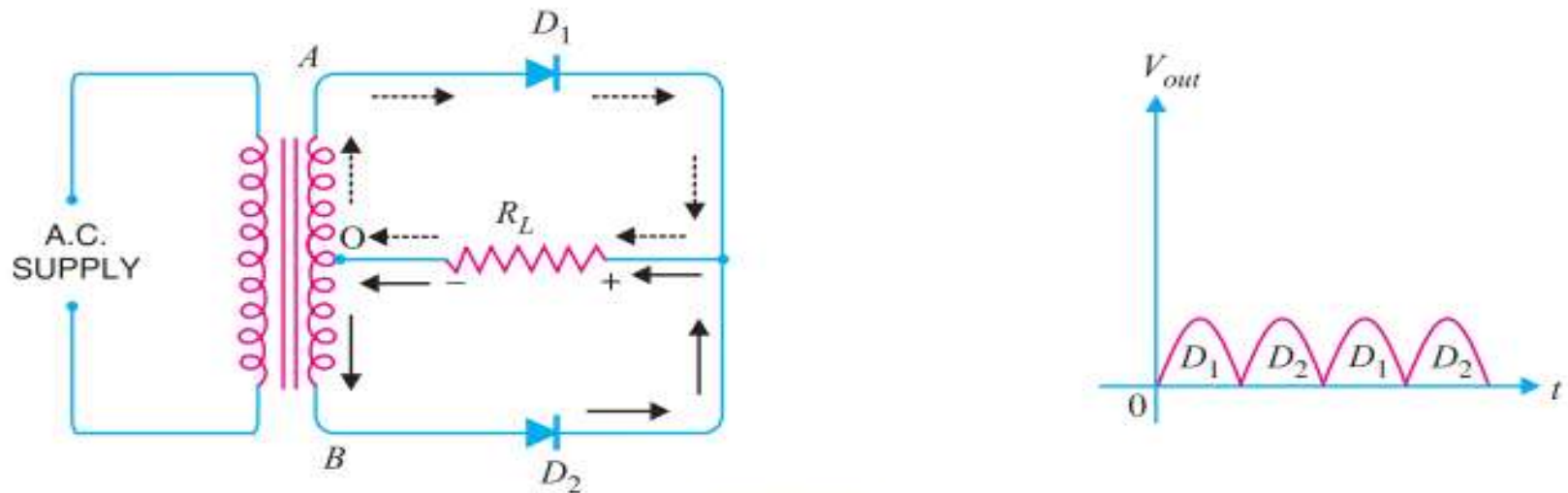





- Circuit has two diodes D_1 , D_2 and a centre tap transformer.
- During positive half cycle Diode D_1 conducts and during negative half cycle Diode D_2 conducts.
- It can be seen that current through load R_L is in the same direction for both cycle.

Full Wave Bridge Rectifier

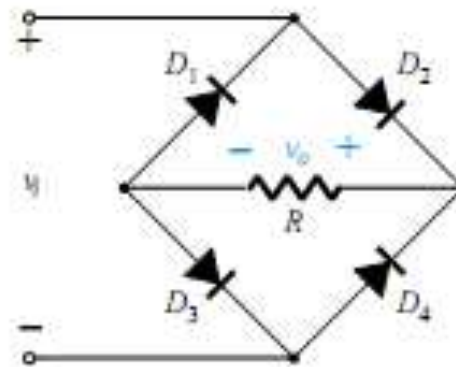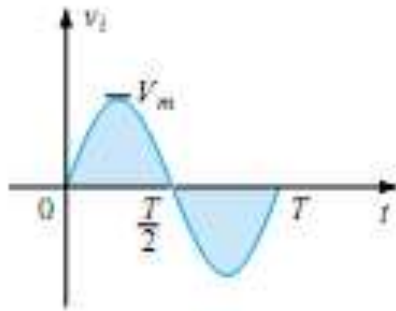


- Need for centre tapped PT is eliminated.
- Consists of 4 diodes instead of 2.

Full Wave Bridge Rectifier

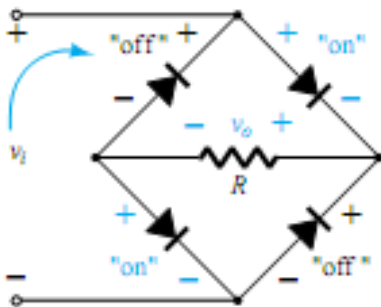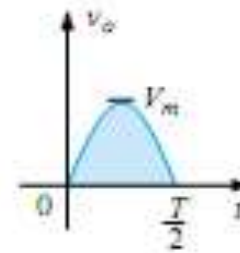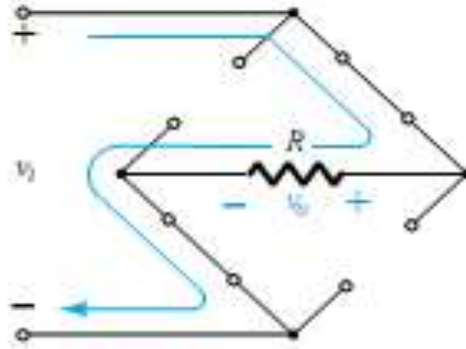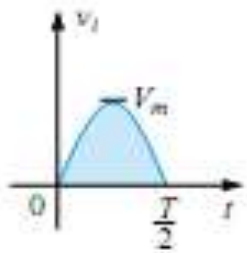


- During period $t=0$ to $t=T/2$ D2 and D3 are conducting while D1 and D4 are in the "off" state.

Full Wave Bridge Rectifier

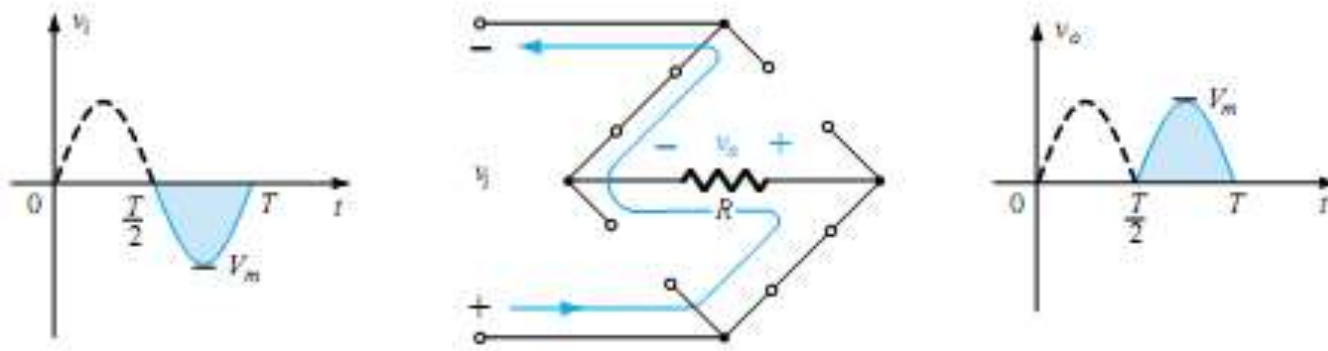

➤ During period $t=T/2$ to $t=T$ D1 and D4 are conducting while D2 and D3 are in the “off” state.

Full Wave Bridge Rectifier

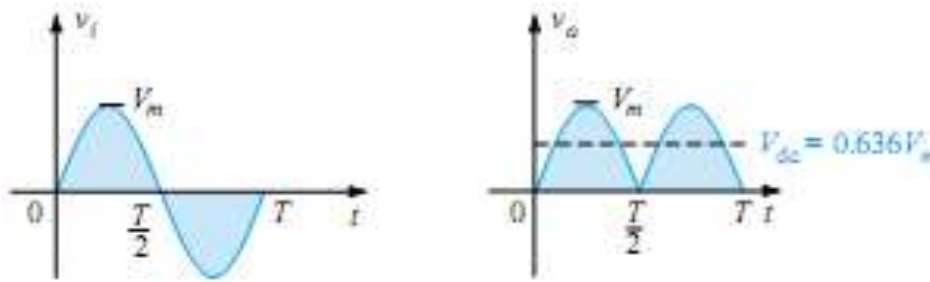


➤ Over one full cycle the input and output voltages will appear as shown in Fig.

$$V_{dc} = 2 * (0.318V_m) = 0.636V_m$$

Full Wave Bridge Rectifier

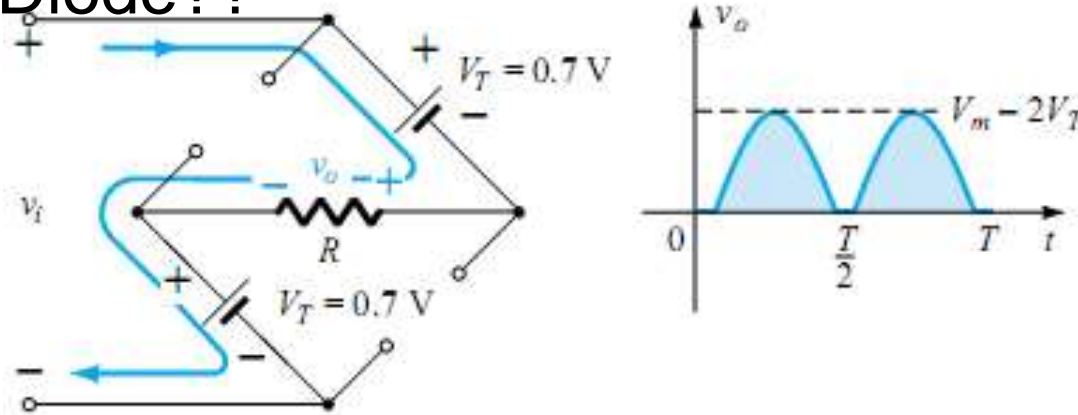What happens if we use silicon Diode instead of ideal Diode??



$$V_{dc} \cong 0.636 (V_m - 2V_T)$$


Full wave Rectifier

□ Output frequency of FWR:

➤ Output frequency of FWR is equal to double of input frequency.

➤ This means when input ac completes one cycle, rectified wave completes two cycle.

$$f_{out} = 2f_{in}$$

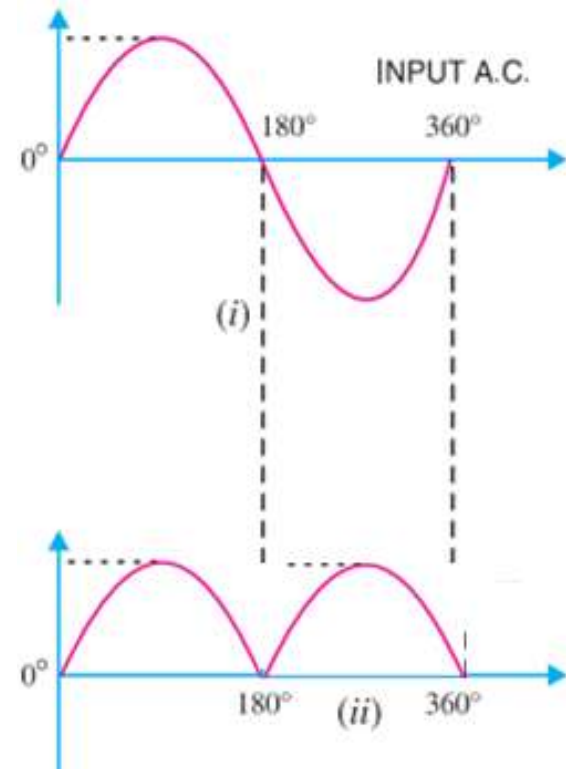

Full Wave Bridge Rectifier

□ Advantage:

- I. Need for centre tap Xformer is eliminated.
- II. PIV is one half of that of centre tap circuit.
- III. Output is twice than that of centre tap circuit.

Disadvantage

- I. Requires 4 diodes.
- II. Internal resistance voltage drop is twice than that of Centre Tap Circuit.

ANY QUSATION?

THANKS TO ALL